

1- Introduction

2- Basic Structures of VHDL

3- Combinational Circuits

4- Sequential Circuits

5- Memory

6- Writing Testbenches

7- Synthesis Issues

8- RTL Cores

4- Sequential Circuits

- **Basic Memory Elements**

- Latch
- D Flip-Flop

- **Registers, Shifters and Counters**

- **State Machine Coding**

- Moore
- Mealy
- Huffman

Basic Memory Elements

- Latch

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY latch1 IS
5      PORT (d, c: IN std_logic; q: OUT std_logic);
6  END latch1;
7
8  ARCHITECTURE behavioral OF latch1 IS
9  BEGIN
10
11      PROCESS (d, c)
12      BEGIN
13          IF c = '1' THEN
14              q <= d;
15          END IF;
16      END PROCESS;
17
18  END ARCHITECTURE behavioral;
```


- Use a process statement for describing a latch
- While c is one, d drives q
- Transparency when c is one

4- Sequential Circuits

Basic Memory Elements

• A Positive-Edge D Flip-Flop
 
```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY DFF1 IS
5      PORT (d, clk: IN std_logic; q : OUT std_logic);
6  END DFF1;
7
8  ARCHITECTURE behavioral OF DFF1 IS
9  BEGIN
10
11      PROCESS (clk)
12      BEGIN
13          IF (clk = '1' AND clk'EVENT) THEN
14              q <= d;
15          END IF;
16      END PROCESS;
17
18  END ARCHITECTURE behavioral;
```




- Detect the edge of the clock and then put d into q
- An event on clk accompanied with $clk=1$, detects the rising edge
- This is a clocked process

4- Sequential Circuits

Basic Memory Elements

• DFF with Synchronous Control

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY DFF1sr IS
5      PORT (d, clk, s, r: IN std_logic; q : OUT std_logic);
6  END DFF1sr;
7
8  ARCHITECTURE behavioral OF DFF1sr IS
9  BEGIN
10
11      PROCESS (clk)
12      BEGIN
13          IF clk = '1' AND clk'EVENT THEN
14              IF s = '1' THEN
15                  q <= '1';
16              ELSIF r = '1' THEN
17                  q <= '0';
18              ELSE
19                  q <= d;
20              END IF;
21          END IF;
22      END PROCESS;
23
24  END ARCHITECTURE behavioral;
```

 


- Use sequential statements in a clocked process to add other functionalities
- This is synchronous control, r, s

4- Sequential Circuits

Basic Memory Elements

- DFF with Asynchronous Control

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY DFF1sr IS
5      PORT (d, clk, s, r: IN std_logic; q : OUT std_logic);
6  END DFF1sr;
7
8  ARCHITECTURE asynchronous OF DFF1sr IS
9  BEGIN
10     PROCESS (clk, s, r) BEGIN
11         IF s = '1' THEN
12             q <= '1';
13         ELSIF r = '1' THEN
14             q <= '0';
15         ELSIF (clk = '1' AND clk'EVENT) THEN
16             q <= d;
17         END IF;
18     END PROCESS;
19 END ARCHITECTURE asynchronous;
```

 

- Implement asynchronous behavior by including corresponding signals in the sensitivity list.
- Clock edge detection becomes the last condition

4- Sequential Circuits

Registers, Shifters and Counters

- Register

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY register8 IS
5  PORT (
6      d      : IN std_logic_vector (7 DOWNT0 0);
7      clk, s, r : IN std_logic;
8      q      : OUT std_logic_vector ( 7 DOWNT0 0));
9  END register8;
10
11 ARCHITECTURE behavioral OF register8 IS
12 BEGIN
13     PROCESS (clk)
14     BEGIN
15         IF (clk = '1' AND clk'EVENT) THEN
16             IF s = '1' THEN
17                 q <= (OTHERS => '1');
18             ELSIF r = '1' THEN
19                 q <= (OTHERS => '0');
20             ELSE
21                 q <= d;
22             END IF;
23         END IF;
24     END PROCESS;
25 END behavioral;
```

- For registers use *std_logic_vector*
- Everything else basically remains the same

4- Sequential Circuits

Registers, Shifters and Counters

- Shift-Registers

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY shift_reg4 IS
5  PORT (
6      d      : IN std_logic_vector (3 DOWNTO 0);
7      clk, ld, rst, l_r, s_in : IN std_logic;
8      q      : OUT std_logic_vector (3 DOWNTO 0));
9  END shift_reg4;
10
11 ARCHITECTURE behavioral OF shift_reg4 IS
12 BEGIN
13     PROCESS (clk)
14         VARIABLE q_t: std_logic_vector (3 DOWNTO 0);
15     BEGIN
16         IF (clk = '1' AND clk'EVENT) THEN
17             IF rst= '1' THEN
18                 q_t := (OTHERS => '0');
19             ELSIF ld = '1' THEN
20                 q_t := d;
21             ELSIF l_r = '1' THEN
22                 q_t := q_t (2 DOWNTO 0) & s_in ;
23             ELSE
24                 q_t := s_in & q_t (3 DOWNTO 1);
25             END IF;
26             q <= q_t;
27         END PROCESS;
28     END behavioral;
```

- Can add functionality such as increment, decrement, shift, etc.
- This is a right/left shift register
- In VHDL cannot use output on RHS, so use a temporary variable

4- Sequential Circuits

Registers, Shifters and Counters

- Counter

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3  USE IEEE.std_logic_unsigned.ALL;
4
5  ENTITY counter4 IS
6  PORT (clk, reset : IN std_logic;
7        count : OUT std_logic_vector (3 DOWNT0 0));
8  END ENTITY;
9
10 ARCHITECTURE procedural OF counter4 IS
11     SIGNAL cnt_reg : std_logic_vector (3 DOWNT0 0);
12 BEGIN
13     PROCESS (clk)
14     BEGIN
15         IF (clk = '1' AND clk'EVENT) THEN
16             IF (reset='1') THEN
17                 cnt_reg <="0000";
18             ELSE
19                 cnt_reg <= cnt_reg + "0001";
20             END IF;
21         END IF;
22     END PROCESS;
23     count <= cnt_reg;
24 END ARCHITECTURE procedural;
```

- Synchronous reset
- Functionality is to increment
- Cannot use output on RHS
- Use a temporary signal, i.e., *cnt_reg*

Registers, Shifters and Counters

- Unconstrained Counter

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3  USE IEEE.std_logic_unsigned.ALL;
4
5  ENTITY counterN IS
6  PORT (clk, reset, load : IN std_logic;
7        d : IN std_logic_vector;
8        count : OUT std_logic_vector);
9  END ENTITY;
10
11  ARCHITECTURE procedural OF counterN IS
12  SIGNAL cnt_reg : std_logic_vector( d'RANGE );
13  BEGIN
14  PROCESS (clk)
15  BEGIN
16  IF (clk = '1' AND clk'EVENT) THEN
17  IF (reset = '1') THEN
18  cnt_reg <= (OTHERS=>'0');
19  ELSIF (load = '1') THEN
20  cnt_reg <= d;
21  ELSE
22  cnt_reg <= cnt_reg + 1;
23  END IF;
24  END IF;
25  END PROCESS;
26  count <= cnt_reg;
27  END ARCHITECTURE procedural;
28
```

- N-bit up counter uses unconstrained vectors
- Size is fixed when instantiated

Registers, Shifters and Counters

- Unconstrained Counter with Generic

```
1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3  USE IEEE.std_logic_unsigned.ALL;
4  USE IEEE.numeric_std.ALL;
5
6  ENTITY counterNupM IS
7      GENERIC( M: integer:=4 );
8      PORT (clk, reset, load : IN std_logic;
9            d : IN std_logic_vector;
10           count : OUT std_logic_vector);
11  END ENTITY;
12
13  ARCHITECTURE procedural OF counterNupM IS
14      SIGNAL cnt_reg : std_logic_vector( d'RANGE );
15  BEGIN
16      PROCESS (clk)
17      BEGIN
18          IF (clk = '1' AND clk'EVENT) THEN
19              IF (reset = '1') THEN
20                  cnt_reg <= (OTHERS=>'0');
21              ELSIF (load = '1') THEN
22                  cnt_reg <= d;
23              ELSE
24                  cnt_reg <= cnt_reg + std_logic_vector(to_unsigned(M, d'length));
25              END IF;
26          END IF;
27      END PROCESS;
28      count <= cnt_reg;
29  END ARCHITECTURE procedural;
```

- Use **generic** for count up
- generic** M will be determined by **generic map** when counter is instantiated

4- Sequential Circuits

Registers, Shifters and Counters

• Unconstrained Counter with C

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3  USE IEEE.std_logic_unsigned.ALL;
4  USE IEEE.numeric_std.ALL;
5
6  ENTITY counterNupM IS
7      GENERIC ( M: integer:=4 );
8      PORT (clk, reset, load : IN std_
9            d : IN std_logic_vector;
10           count : OUT std_logic_vect
11  END ENTITY;


```

```

        uut: ENTITY WORK.counterNupM
            GENERIC MAP ( M => 3)
            PORT MAP (
                clk => clk,
                reset => reset,
                load => load,
                d => "00010",
                count => count
            );

```

 - Use **generic** for count up
- **generic** *M* will be determined by **generic map** when counter is instantiated




```

21  ELSIF (load = '1') THEN
22      cnt_reg <= d;
23  ELSE
24      cnt_reg <= cnt_reg + std_logic_vector(to_unsigned(M, d'length));
25  END IF;
26  END IF;
27  END PROCESS;
28  count <= cnt_reg;
29  END ARCHITECTURE procedural;

```

State Machines

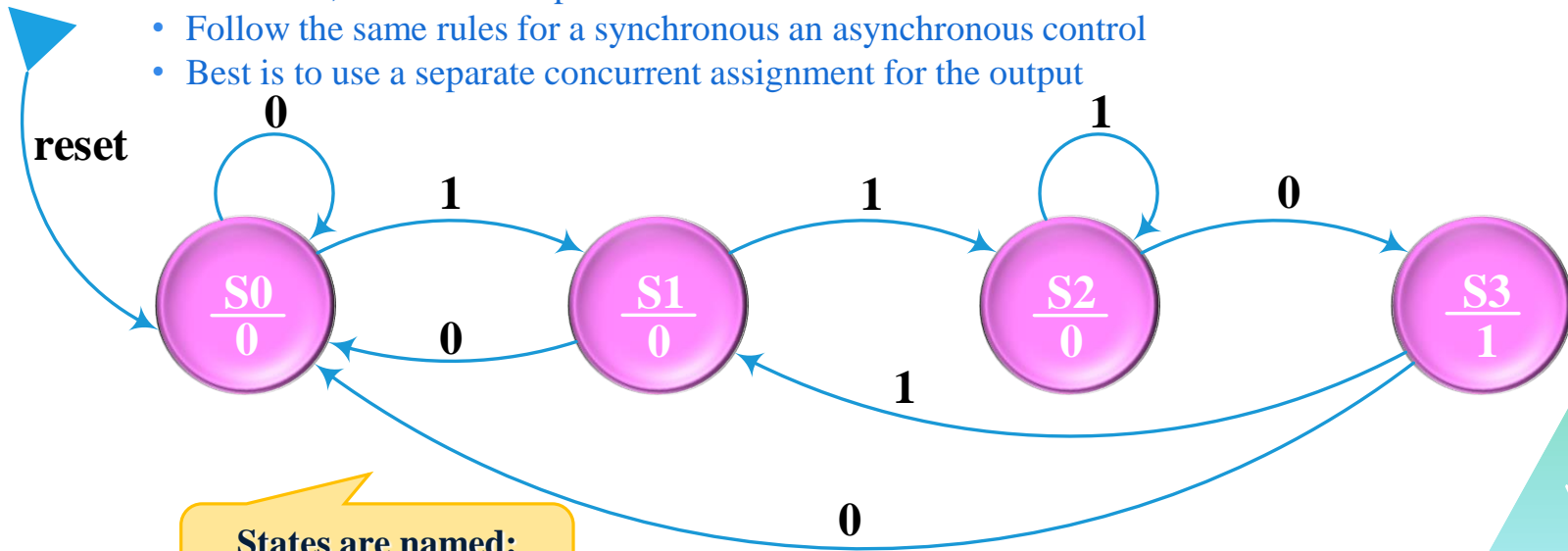- **A Moore Machine 110 Sequence Detector**
- Define states by an enumeration type
- As before, use a clocked process
- Follow the same rules for a synchronous and asynchronous control
- Best is to use a separate concurrent assignment for the output




States are named:
s0 , s1 , s2 , s3

4- Sequential Circuits

State Machines

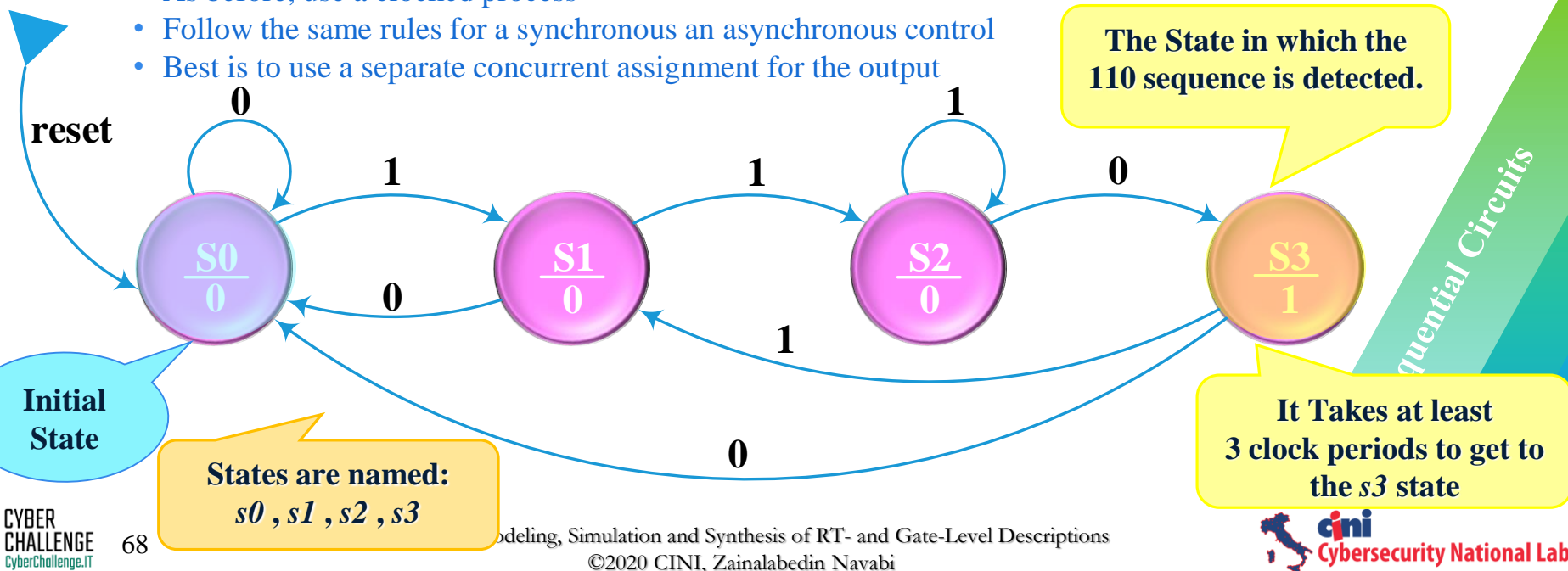
- **A Moore Machine 110 Sequence Detector**
- Define states by an enumeration type
- As before, use a clocked process
- Follow the same rules for a synchronous and asynchronous control
- Best is to use a separate concurrent assignment for the output



State Machines

• A Moore Machine 110 Sequence Detector

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY detector110 IS
5      PORT (a, clk, reset : IN std_logic; w : OUT std_logic);
6  END ENTITY;
7
8  ARCHITECTURE procedural OF detector110 IS
9      TYPE state IS (S0, S1, S2, S3);
10     SIGNAL current : state := S0;
11 BEGIN
12     PROCESS (clk) BEGIN
13         IF (clk = '1' AND clk'EVENT) THEN
14             IF reset = '1' THEN current <= S0;
15             ELSE
16                 CASE current IS
17                     WHEN S0 =>
18                         IF a='1' THEN current <= S1;
19                         ELSE current <= S0; END IF;
```

 

- Declare *current* as the register that holds the FSM state; two bits
- Use a process statement for transitions
- Use a signal assignment for the output
- Can use a process statement for the output if output is more complex


4-Sequential Circuits
State Machines

State Machines

• A Moore Machine 110 Sequence Detector

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY detector110 IS
5      PORT (a, clk, reset : IN std_logic; w : OUT std_logic);
6  END ENTITY;
7
8  ARCHITECTURE procedural OF detector110 IS
9
10     TYPE s
11     SIGNAL
12 BEGIN
13     PROCESS
14         IF
15
16
17
18
19
20     WHEN S1 =>
21         IF a='1' THEN current <= S2;
22         ELSE current <= S0; END IF;
23     WHEN S2 =>
24         IF a='1' THEN current <= S2;
25         ELSE current <= S3; END IF;
26     WHEN S3 =>
27         IF a='1' THEN current <= S1;
28         ELSE current <= S0; END IF;
29     WHEN OTHERS => current <= S0;
30     END CASE;
31     END IF;
32     END IF;
33     END PROCESS;
34     w <= '1' WHEN current = S3 ELSE '0';
35 END ARCHITECTURE procedural;
    
```

 


- Declare *current* as the register that holds the FSM state; two bits
- Use a process statement for transitions
- Use a signal assignment for the output
- Can use a process statement for the output if output is more complex

4-Sequential Circuits
State Machines

State Machines

 - **A Mealy Machine 1101 Sequence Detector**
- Output is issued on the edges
- Use the same coding style




4- Sequential Circuits
State Machines

State Machines

• A Mealy Machine 1101 Sequence Detector

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY detector1101 IS
5      PORT (a, clk, reset : IN std_logic; w : OUT std_logic);
6  END ENTITY;
7
8  ARCHITECTURE procedural OF detector1101 IS
9      TYPE state IS (S0, S1, S2, S3);
10     SIGNAL current : state := S0;
11 BEGIN
12     PROCESS (clk) BEGIN
13         IF (clk = '0' AND clk'EVENT) THEN
14             IF reset = '1' THEN current <= S0;
15             ELSE
16                 CASE current IS
17                     WHEN S0 =>
18                         IF a='1' THEN current <= S1;
19                         ELSE current <= S0; END IF;
```

 

- Use the same style as registers and counters
- Use a clocked process
- Synchronous/Asynchronous control rules are applied
- A separate concurrent process is used for output


4- Sequential Circuits
State Machines

State Machines

• A Mealy Machine 1101 Sequence Detector

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY detector1101 IS
5      PORT (a, clk, reset : IN std_logic; w : OUT std_logic);
6  END ENTITY;
```

```
7
8  20      WHEN S1 =>
9      21          IF a='1' THEN current <= S2;
10     22          ELSE current <= S0; END IF;
11     23      WHEN S2 =>
12     24          IF a='1' THEN current <= S2;
13     25          ELSE current <= S3; END IF;
14     26      WHEN S3 =>
15     27          IF a='1' THEN current <= S1;
16     28          ELSE current <= S0; END IF;
17     29      WHEN OTHERS => current <= S0;
18     30      END CASE;
19     31      END IF;
20     32      END IF;
21     33      END PROCESS;
22     34      w <= '1' WHEN (current = S3 AND a='1') ELSE '0';
23     35  END ARCHITECTURE procedural;
```

 

- Use the same style as registers and counters
- Use a clock process
- Synchronous/Asynchronous control rules are applied
- A separate concurrent process is used for output

4-Sequential Circuits
State Machines

State Machines

- **Mealy vs. Moore**

Moore Machine

1. Output depends on the present state only
2. Input changes between clock don't propagate to the output
3. Generally, it has more states than Mealy
4. It reacts slower to inputs (One clock cycle later)
5. Output is always synchronous with the clock


Mealy Machine

1. Output depends on the present state and present input
2. Synchronous input changes can propagate to the output
3. Generally, it has fewer states than Moore Machine
4. They react faster to inputs
5. Asynchronous output generation

- Don't use mealy unless its input comes from a circuit synchronized with the same clock

4- Sequential Circuits
State Machine


State Machines - Huffman Model

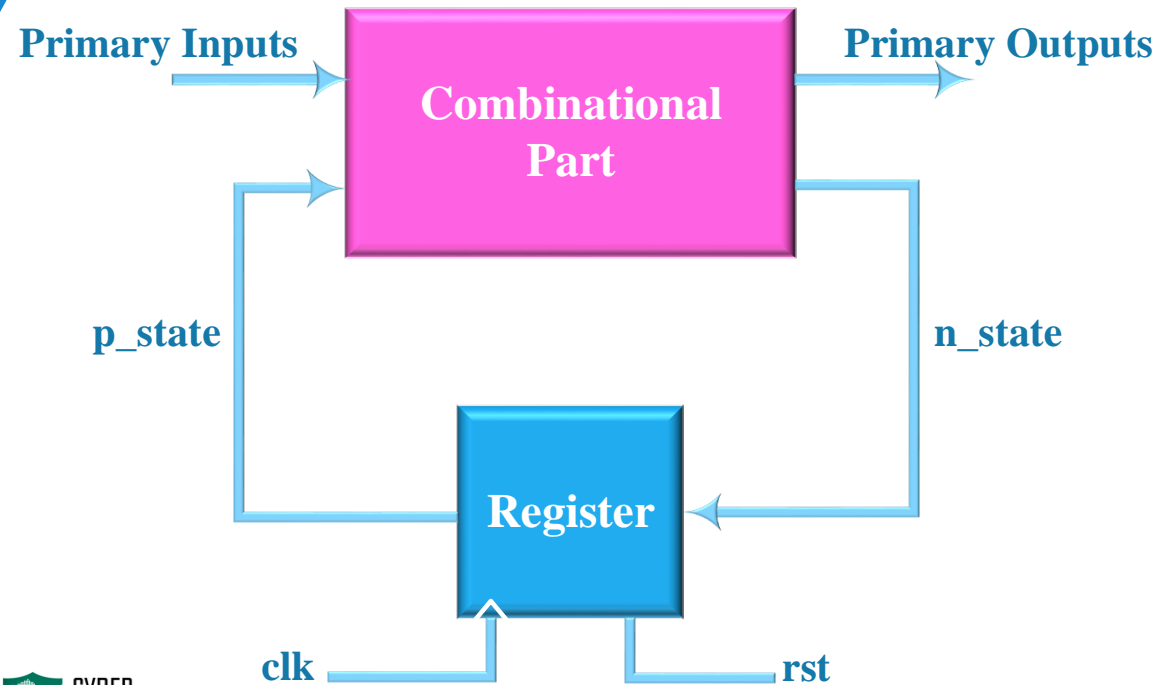

- A better coding style for sequential circuit; separates combinational and sequential parts
- This is called Huffman model
- Alternatively, can further separate outputs from transitions

4- Sequential Circuits
State Machines


State Machines - Huffman Model

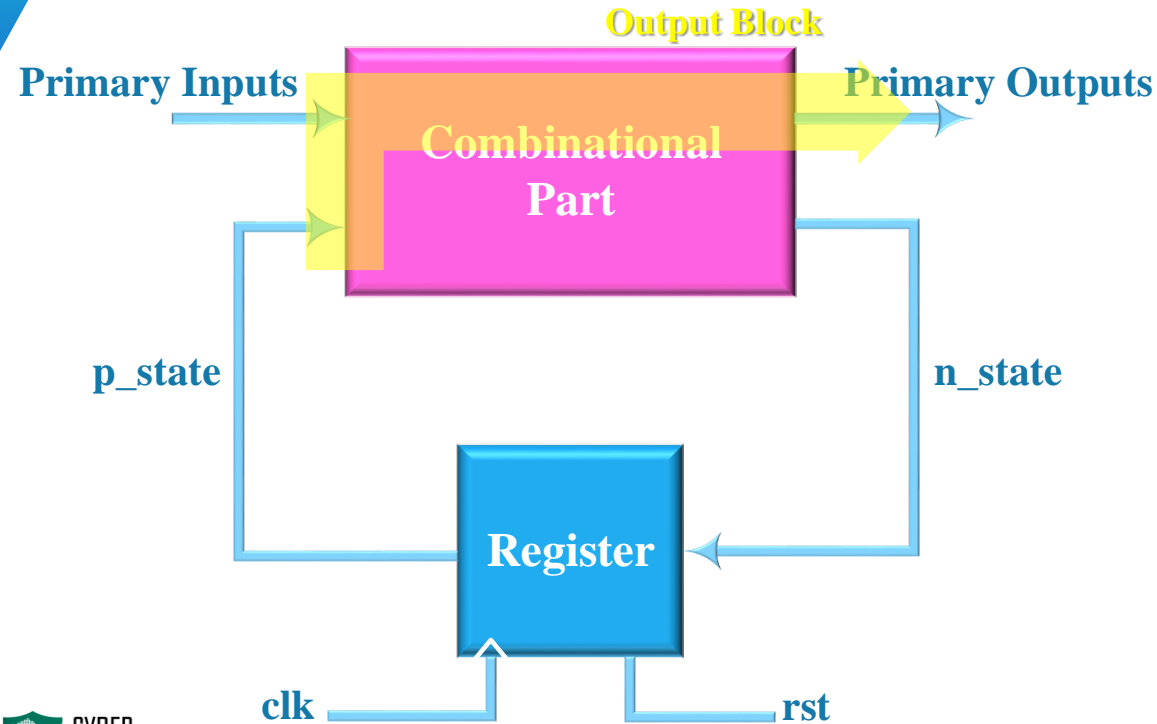

- A better coding style for sequential circuit; separates combinational and sequential parts
- This is called Huffman model
- Alternatively, can further separate outputs from transitions

4- Sequential Circuits
State Machines

State Machines - Huffman Model

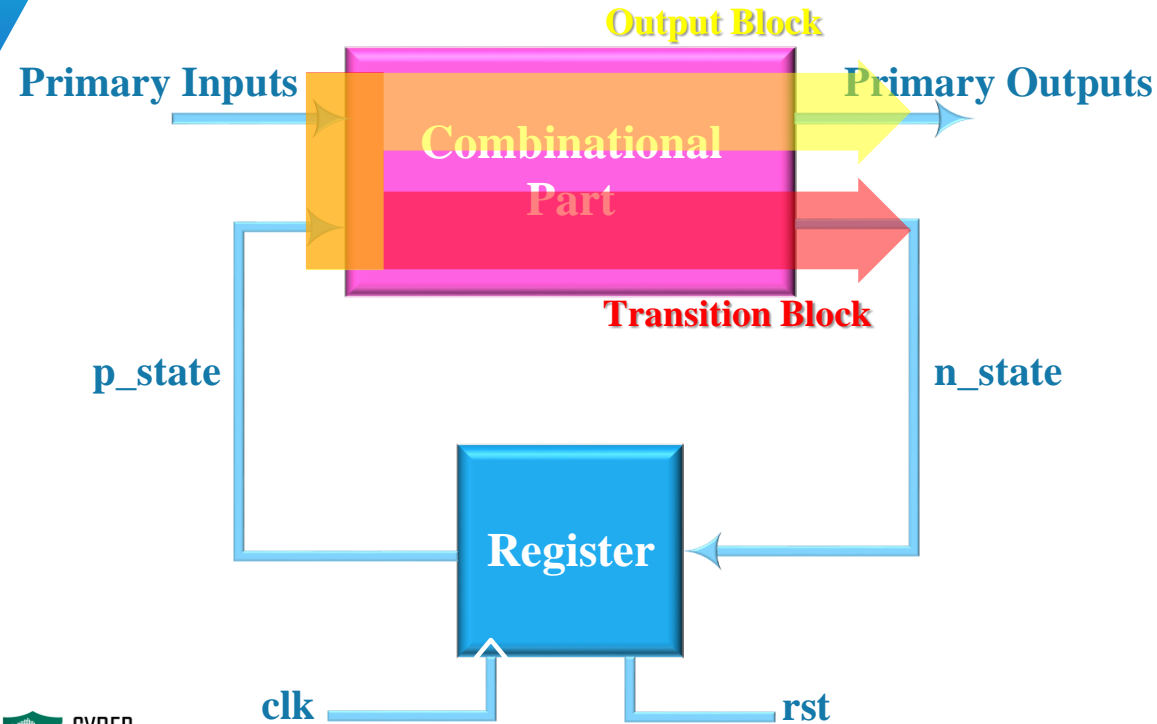

- A better coding style for sequential circuit; separates combinational and sequential parts
- This is called Huffman model
- Alternatively, can further separate outputs from transitions


4- Sequential Circuits
State Machines

Huffman Model

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  ENTITY moore_detector IS
5      PORT (a, rst, clk : IN std_logic; w : OUT std_logic);
6  END ENTITY ;
7
8  ARCHITECTURE procedural OF moore_detector IS
9      TYPE state IS (S0, S1, S2, S3);
10     SIGNAL p_state, n_state : state;

```

 

- The same Moore detector using Huffman
- All combinational inputs appear on the sensitivity list
- All combinational outputs receive a value no matter what
- The register block is just a clocked process


4- Sequential Circuits
State Machines

Huffman Model

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;
3
4  13  combinational: PROCESS (p_state, a) BEGIN
5
6      14      n_state <= S0;
7
8      15      w <= '0';
9
10     16      CASE p_state IS
11
12         WHEN S0 =>
13             IF a='1' THEN n_state <= S1;
14             ELSE n_state <= S0; END IF;
15             w <= '0';
16
17         WHEN S1 =>
18             IF a='1' THEN n_state <= S2;
19             ELSE n_state <= S0; END IF;
20             w <= '0';
21
22         WHEN S2 =>
23             IF a='1' THEN n_state <= S2;
24             ELSE n_state <= S3; END IF;
25             w <= '0';
26
27         WHEN S3 =>
28             IF a='1' THEN n_state <= S1;
29             IF a='1' THEN n_state <= S1;
30             ELSE n_state <= S0; END IF;
31             w <= '1';
32
33         WHEN OTHERS => n_state <= S0;
34
35     END CASE;
36
37 END PROCESS combinational;

```

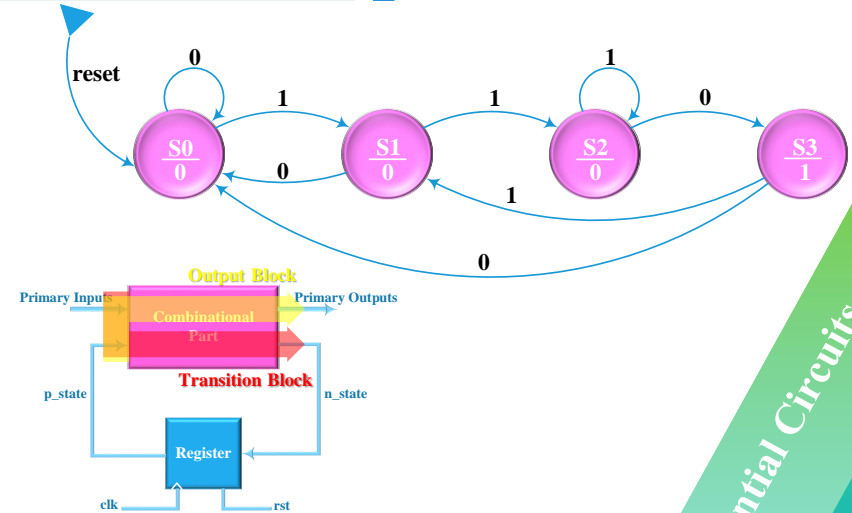

- The same Moore detector using Huffman
- All combinational inputs appear on the sensitivity list
- All combinational outputs receive a value no matter what
- The register block is just a clocked process

4- Sequential Circuits
State Machines

Huffman Model

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.ALL;


13 combinational: PROCESS (p_state, a) BEGIN
14     n_state <= S0;

38 sequential: PROCESS (clk) BEGIN
39     IF (clk = '1' AND clk'EVENT) THEN
40         IF rst = '1' THEN
41             p_state <= S0;
42         ELSE
43             p_state <= n_state;
44         END IF;
45     END IF;
46 END PROCESS sequential;

48 END ARCHITECTURE;

28     w <= '0';
29     WHEN S3 =>
30         IF a='1' THEN n_state <= S1;
31         IF a='1' THEN n_state <= S1;
32         ELSE n_state <= S0; END IF;
33         w <= '1';
34     WHEN OTHERS => n_state <= S0;
35 END CASE;
36 END PROCESS combinational;

```

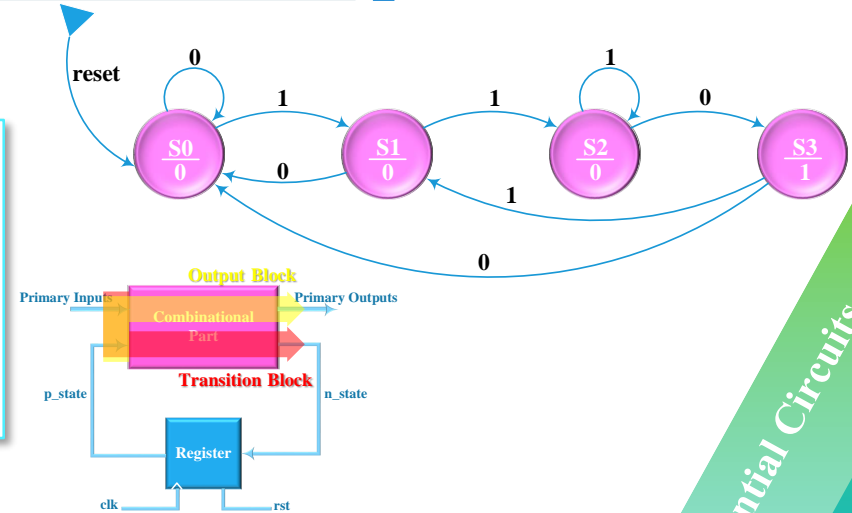


- The same Moore detector using Huffman
- All combinational inputs appear on the sensitivity list
- All combinational outputs receive a value no matter what
- The register block is just a clocked process

4- Sequential Circuits
State Machines

Huffman Model

- A More Modular Moore State Machine Style for 110 Sequence Detector
 
```
1  LIBRARY IEEE;  
2  USE IEEE.std_logic_1164.ALL;  
3  
4  ENTITY moore_modular IS  
5      PORT (a, clk, rst : IN std_logic; w : OUT std_logic);  
6  END ENTITY moore_modular;  
7  
8  ARCHITECTURE procedural OF moore_modular IS  
9      TYPE state IS (S0, S1, S2, S3);  
10     SIGNAL p_state, n_state : state;
```




4-Sequential Circuits
State Machines

- Separate output from transition

Huffman Model

- A More Modular Moore State Machine Style for 110 Sequence Detector

```
1  LIBRARY IEEE;  
2  USE WORKING_AREA_1 ALL;  
3  
4  BEGIN  
5  
6  PROCESS (p_state, a) BEGIN  
7      CASE p_state IS  
8          WHEN S0 =>  
9              IF a='1' THEN n_state <= S1;  
10             ELSE n_state <= S0; END IF;  
11          WHEN S1 =>  
12              IF a='1' THEN n_state <= S2;  
13              ELSE n_state <= S0; END IF;  
14          WHEN S2 =>  
15              IF a='1' THEN n_state <= S2;  
16              ELSE n_state <= S3; END IF;  
17          WHEN S3 =>  
18              IF a='1' THEN n_state <= S1;  
19              ELSE n_state <= S0; END IF;  
20          WHEN OTHERS => n_state <= S0;  
21      END CASE;  
22  END PROCESS;
```

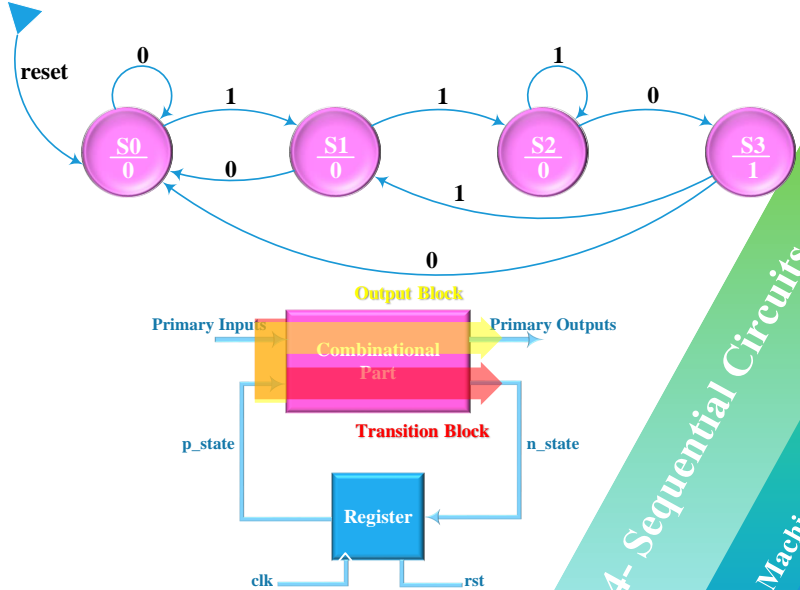


- Separate output from transition

Huffman Model

- A More Modular Moore State Machine Style for 110 Sequence Detector

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY Huffman IS
5      PORT (a: IN STD_LOGIC;
6            reset: IN STD_LOGIC;
7            clk: IN STD_LOGIC;
8            rst: IN STD_LOGIC;
9            p_state: IN STD_LOGIC;
10             n_state: OUT STD_LOGIC);
11 END ENTITY Huffman;
12
13 BEGIN
14     PROCESS (p_state, a) BEGIN
15         CASE p_state IS
16             WHEN S0 =>
17                 IF a='1' THEN n_state <= S1;
18                 ELSE n_state <= S0; END IF;
19             WHEN S1 =>
20                 IF a='1' THEN n_state <= S2;
21                 ELSE n_state <= S0; END IF;
22             WHEN S2 =>
23                 IF a='1' THEN n_state <= S2;
24                 ELSE n_state <= S3; END IF;
25             WHEN S3 =>
26                 IF a='1' THEN n_state <= S1;
27                 ELSE n_state <= S0; END IF;
28             WHEN OTHERS => n_state <= S0;
29         END CASE;
30     END PROCESS;
```

 


4- Sequential Circuits
State Machines

- Separate output from transition

Huffman Model

- A More Modular Moore State Machine Style for 110 Sequence Detector

```
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY Huffman IS
5      PORT (w: IN STD_LOGIC;
6            rst: IN STD_LOGIC);
7  END ENTITY Huffman;
8
9  ARCHITECTURE Huffman OF Huffman IS
10
11      BEGIN
12
13          PROCESS (p_state, a) BEGIN
14              CASE p_state IS
15                  WHEN S0 => w <= '0';
16                  WHEN S1 => w <= '0';
17                  WHEN S2 => w <= '0';
18                  WHEN S3 => w <= '1';
19                  WHEN OTHERS => w <= '0';
20              END CASE;
21          END PROCESS;
22
23          sequential: PROCESS (clk) BEGIN
24              IF (clk = '1' AND clk'EVENT) THEN
25                  IF rst = '1' THEN
26                      p_state <= S0;
27                  ELSE
28                      p_state <= n_state;
29                  END IF;
30              END IF;
31          END PROCESS sequential;
32      END ARCHITECTURE;
```

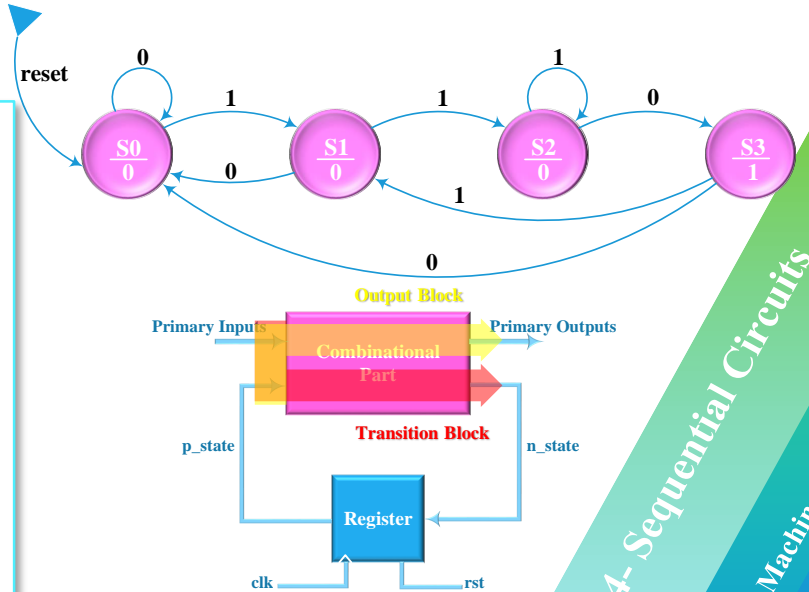

4- Sequential Circuits
State Machines

- Separate output from transition


Huffman Model

- A More Modular Moore State Machine Style for 110 Sequence Detector

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY Huffman IS
5      PORT (w: IN STD_LOGIC;
6            rst: IN STD_LOGIC;
7            clk: IN STD_LOGIC);
8  END ENTITY Huffman;
9
10 ARCHITECTURE Huffman OF Huffman IS
11     BEGIN
12
13         PROCESS (p_state, a) BEGIN
14             CASE p_state IS
15                 WHEN S0 => w <= '0';
16                 WHEN S1 => w <= '0';
17                 WHEN S2 => w <= '0';
18                 WHEN S3 => w <= '1';
19                 WHEN OTHERS => w <= '0';
20             END CASE;
21         END PROCESS;
22
23         sequential: PROCESS (clk) BEGIN
24             IF (clk = '1' AND clk'EVENT) THEN
25                 IF rst = '1' THEN
26                     p_state <= S0;
27                 ELSE
28                     p_state <= n_state;
29                 END IF;
30             END IF;
31         END PROCESS sequential;
32     END ARCHITECTURE;

```

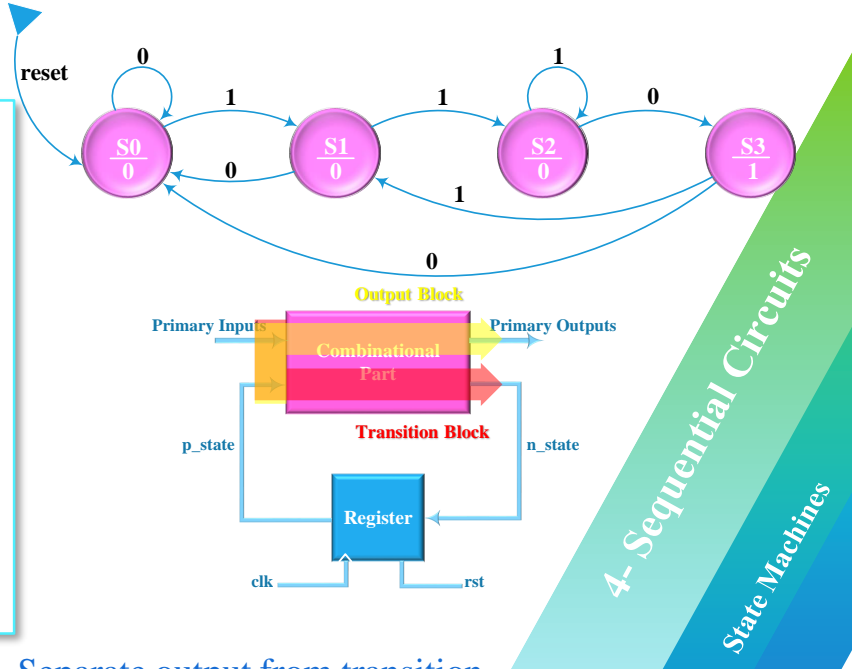

- Separate output from transition