

Logic Gates & Flip-Flops

1

Paolo PRINETTO

Director
CINI Cybersecurity
National Laboratory
Paolo.Prinetto@polito.it
Mob. +39 335 227529



<https://cybersecnatlab.it>

License & Disclaimer

2

License Information

This presentation is licensed under the Creative Commons BY-NC License



To view a copy of the license, visit:

<http://creativecommons.org/licenses/by-nc/3.0/legalcode>

Disclaimer


- We disclaim any warranties or representations as to the accuracy or completeness of this material.
- Materials are provided “as is” without warranty of any kind, either express or implied, including without limitation, warranties of merchantability, fitness for a particular purpose, and non-infringement.
- Under no circumstances shall we be liable for any loss, damage, liability or expense incurred or suffered which is claimed to have resulted from use of this material.

Prerequisites

- Students are assumed to be familiar with:
 - Lecture:
 - *HW_S_2 – Hardware Systems Representations*
 - The basic concepts, postulates, and theorems of Boolean Algebras.

Further readings

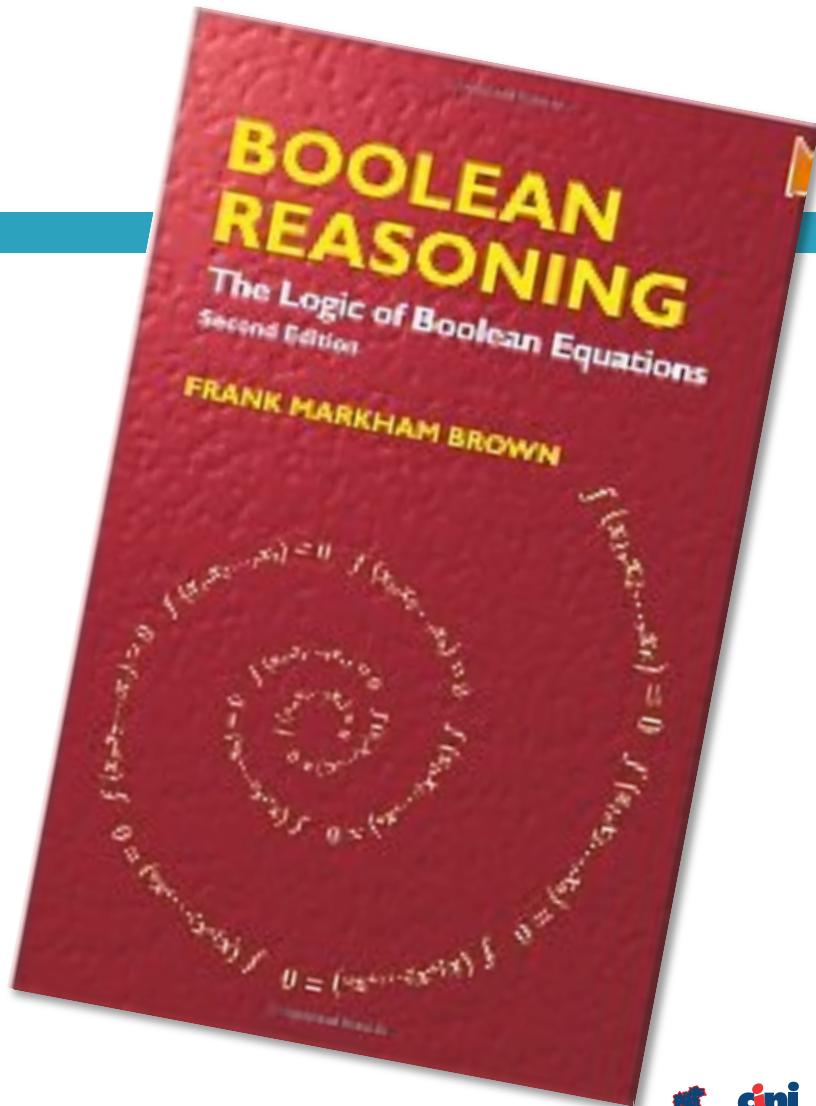- Students interested in a deeper knowledge of the arguments covered in this lecture can refer, for instance, to:




Goal

5

- This lecture presents the set of devices usually considered as “elementary” at the Structural domain of the Logic level abstraction, i.e., *Logic Gates* and *Flip-Flops*.

Structural domain – Logic level

Abstraction levels
PE
RT
Logic
Device

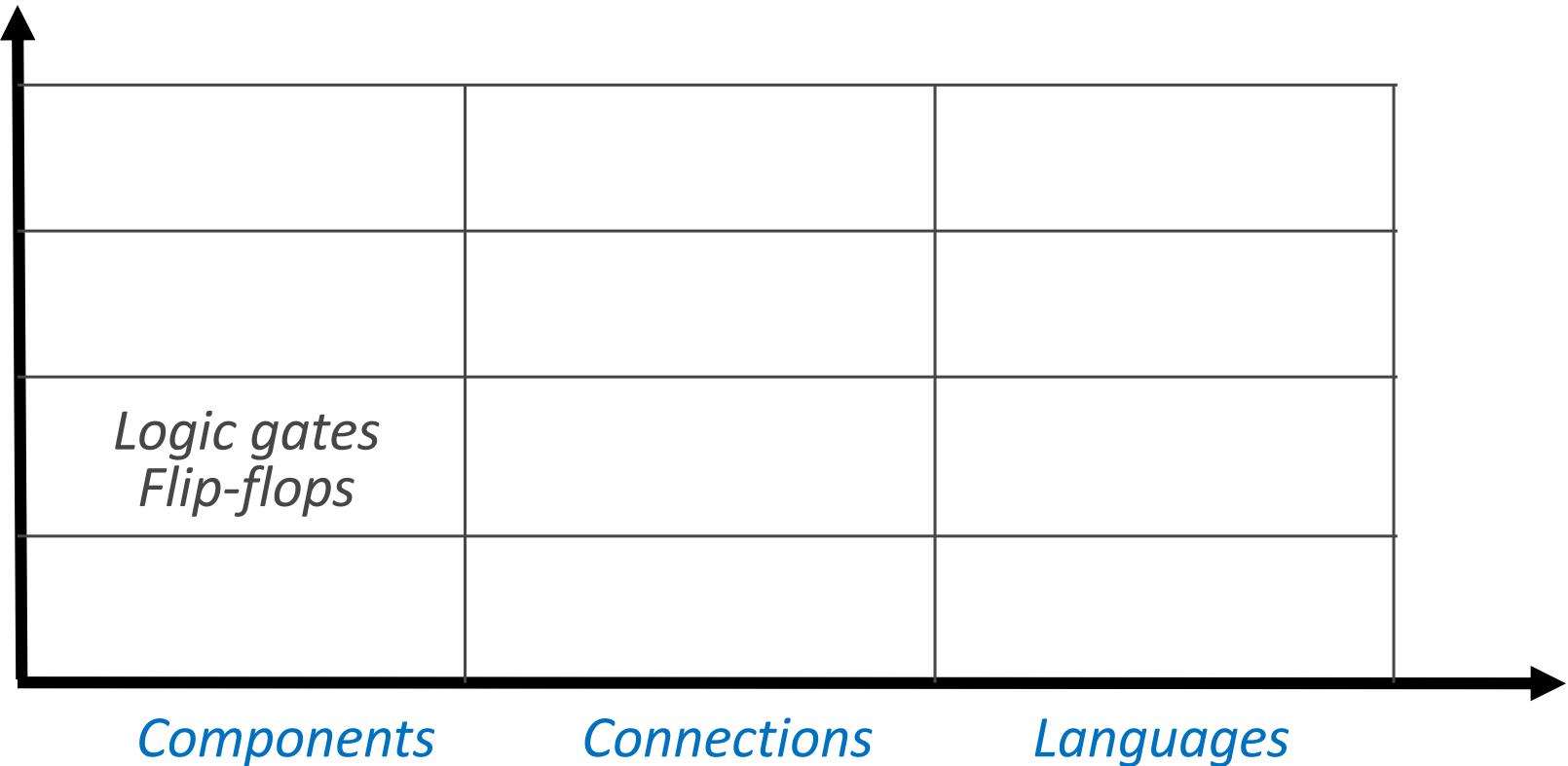

Outline

7

- Combinational devices:
 - Basic Boolean Functions & Logic Gates
- Sequential devices:
 - Flip-Flops
 - Scannable Flip-Flops

Outline

8

- Combinational devices:
 - Basic Boolean Functions & Logic Gates
- Sequential devices:
 - Flip-Flops
 - Scannable Flip-Flops

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

Why are they so significant?

- Electronic devices (often referred to as *Logic Gates*) are available to implement each of these basic boolean functions
- Each device is usually given the same name of the corresponding boolean functions, e.g.:

AND function \Leftrightarrow AND gate

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“Logic Complement” or “NOT” function

Informal definition

- The NOT function is a unary function, providing the logic complement of its input variable.

Representations

- x'
- \bar{x}
- $\text{not}(x)$

“Logic Complement” or “NOT” function

13

Axiomatic definition

$$0' = 1$$

$$1' = 0$$

$$\text{not}(0) = 1$$

$$\text{not}(1) = 0$$

Truth table

x	not(x)
0	1
1	0

“Logic Complement” or “NOT” function

14

Functional definition


```
if x = 1  
    then not(x) = 0  
    else not(x) = 1  
  
endif
```

Theorems


- $(x')' = x$
- $\text{not}(\text{not}(x)) = x$

NOT gate, or inverter

traditional symbol

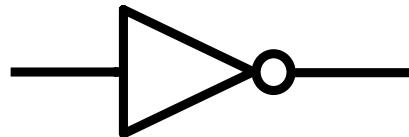

IEEE symbol

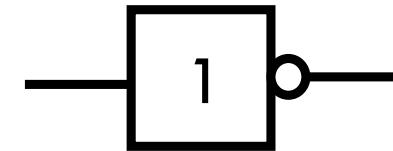

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“Logic product” or “AND” function

Informal definition

- The AND function on 2 (or more) input variables provides the value 1 iff *all* its input variables get the value 1.

Representations

- $x \cdot y$
- $x \; y$
- $\text{and} (x, y)$

“Logic product” or “AND” function

18

Axiomatic definition

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$\text{and}(0,0) = 0$$

$$\text{and}(0,1) = 0$$

$$\text{and}(1,0) = 0$$

$$\text{and}(1,1) = 1$$

Truth table

x	y	and(x,y)
0	0	0
0	1	0
1	0	0
1	1	1

“Logic product” or “AND” function

19

Functional definition

```
if x = 1  
  then and(x, y) = y  
  else and(x, y) = 0  
endif
```

Theorems


- $x \cdot 0 = 0$
- $x \cdot 1 = x$
- $x \cdot x = x$
- $x \cdot x' = 0$
- $x \cdot y = y \cdot x$
- $x \cdot y \cdot z = (x \cdot y) \cdot z = x \cdot (y \cdot z)$

“Logic product” or “AND” function

traditional symbol



IEEE symbol

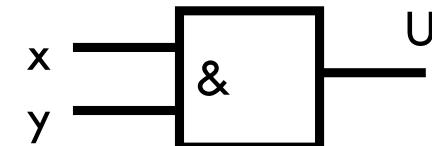

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“Logic sum” or “OR” function

Informal definition

- The OR function on 2 (or more) input variables provides the value 1 iff *at least one* of its input variables gets the value 1.

Representations

- $x + y$
- $\text{or}(x,y)$

8. A logician's wife is having a baby. The doctor immediately hands the newborn to the dad.

His wife asks impatiently: "So, is it a boy or a girl" ?

The logician replies: "yes".

“Logic sum” or “OR” function

24

Axiomatic definition

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$\text{or}(0,0) = 0$$

$$\text{or}(0,1) = 1$$

$$\text{or}(1,0) = 1$$

$$\text{or}(1,1) = 1$$

Truth table

x	y	$\text{or}(x,y)$
0	0	0
0	1	1
1	0	1
1	1	1

“Logic sum” or “OR” function

25

Functional definition


```
if x = 1  
  then or(x, y) = 1  
  else or(x, y) = y  
endif
```

Theorems


- $x + 0 = x$
- $x + 1 = 1$
- $x + x = x$
- $x + x' = 1$
- $x + y = y + x$
- $x + y + z = (x + y) + z = x + (y + z)$

“Logic sum” or “OR” function

traditional symbol

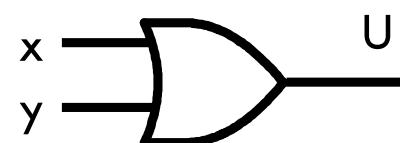

IEEE symbol

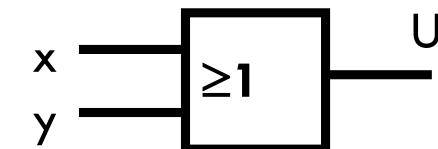

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“NAND” function

Informal definition

- The NAND function on 2 (or more) input variables provides the value 1 iff *at least one* of its input variables get the value 0.

Representations

- `nand (x, y)`

“NAND” function

29

Axiomatic definition

$$\text{nand}(0,0) = 1$$

$$\text{nand}(0,1) = 1$$

$$\text{nand}(1,0) = 1$$

$$\text{nand}(1,1) = 0$$

Truth table

x	y	nand(x,y)
0	0	1
0	1	1
1	0	1
1	1	0

“NAND” function

30

Functional definition

```
if x = 1  
    then nand(x, y) = not(y)  
    else nand(x, y) = 1  
endif
```

Theorems


- $\text{nand}(x, 0) = 1$
- $\text{nand}(x, 1) = x'$
- $\text{nand}(x, x) = x'$
- $\text{nand}(x, x') = 1$
- $\text{nand}(x, y) = \text{nand}(y, x)$
- $\text{nand}(x, y) = \text{not}(\text{and}(x, y))$
- $\text{nand}(x, y, z) = \text{nand}(x, \text{and}(y, z)) =$
 $= \text{nand}(\text{and}(x, y), z) = \text{nand}(x, \text{and}(y, z))$

“NAND” function

traditional symbol



IEEE symbol

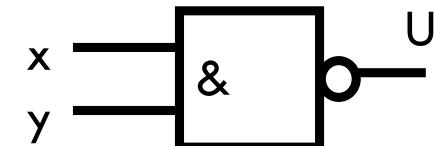

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“NOR” function

Informal definition

- The NOR function on 2 (or more) input variables provides the value 1 iff *none* of its input variables get the value 0.

Representations

- $\text{nor} (x, y)$

“NOR” function

34

Axiomatic definition

$$\text{nor}(0,0) = 1$$

$$\text{nor}(0,1) = 0$$

$$\text{nor}(1,0) = 0$$

$$\text{nor}(1,1) = 1$$

Truth table

x	y	nor(x,y)
0	0	1
0	1	0
1	0	0
1	1	0

“NOR” function

35

Functional definition


```
if x = 1  
  then nor(x, y) = 0  
else nor(x, y) = not(y)  
endif
```

Theorems


- $\text{nor}(x, 0) = x'$
- $\text{nor}(x, 1) = 0$
- $\text{nor}(x, x) = x'$
- $\text{nor}(x, x') = 0$
- $\text{nor}(x, y) = \text{nor}(y, x)$
- $\text{nor}(x, y) = \text{not}(\text{or}(x, y))$
- $\text{nor}(x, y, z) = \text{nor}(x, \text{or}(y, z)) =$
 $= \text{nor}(\text{or}(x, y), z) = \text{nor}(x, \text{or}(y, z))$

“NOR” function

traditional symbol

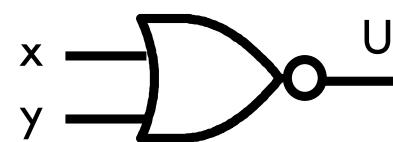

IEEE symbol

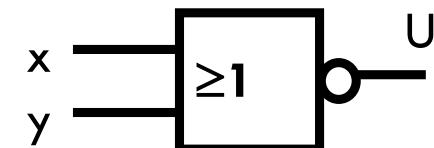

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - exnor

“EXOR” function

Informal definition

- The EXOR function on 2 (or more) input variables provides the value 1 iff *an odd #* of its input variables get the value 1.

Representations

- $x \oplus y$
- $\text{exor}(x,y)$
- $\text{xor}(x,y)$

“EXOR” function

39

Axiomatic definition

$$0 \oplus 0 = 0$$

$$0 \oplus 1 = 1$$

$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$

Truth table

x	y	exor(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

“EXOR” function

40

Functional definition #1

```
if x = 1  
    then exor(x,y) = not(y)  
else exor(x,y) = y  
endif
```

Remark

The exor function can be seen as a *controlled inverter*:

x	y	exor(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

“EXOR” function

41

Functional definition #2

```
if x = y  
    then exor(x,y)=0  
else exor(x,y)=1  
endif
```

Remark

The exor function can be seen as a *comparator*:

x	y	exor(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

“EXOR” function

42

Functional definition #3

```
if (x+y) mod 2 =0  
    then exor(x,y)=0  
else exor(x,y)=1  
endif
```

Remark

The exor function can be seen as a *modulo 2 adder*:


x	y	exor(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

“EXOR” function

traditional symbol



IEEE symbol

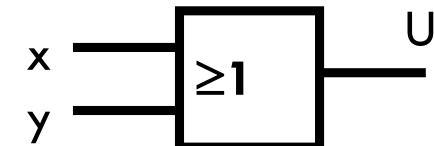

“EXOR” function

Theorems

- $\text{exor}(x, 0) = x$
- $\text{exor}(x, 1) = x'$
- $\text{exor}(x, x) = 0$
- $\text{exor}(x, x') = 1$
- $\text{exor}(x, y) = \text{exor}(y, x)$
- $\text{exor}(x, y) = \text{exor}(x', y')$
- $\text{exor}(x, y') = \text{exor}(x', y) = (\text{exor}(x,y))'$
- $\text{exor}(x, y) = xy' + x'y = (xy)'(x+y)$

Composition

$$\begin{aligned}\text{exor}(x, y, z) &= \text{exor}(x, \text{exor}(y, z)) = \\ &= \text{exor}(\text{exor}(x, y), z)\end{aligned}$$


“EXOR” function

Composition


When using 2-input exor gates to implement N-input exor functions, 2 solutions are possible

“EXOR” function

Example

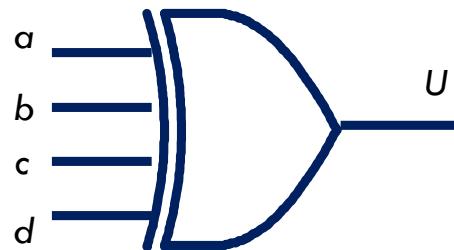


1st solution

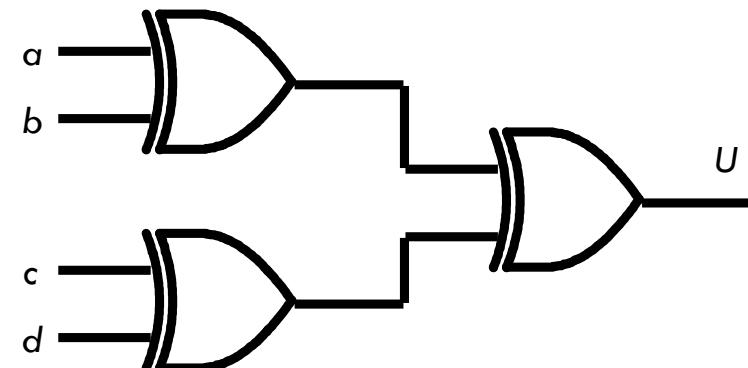


- Delay: $O(\log n)$
- Cost: $O(n)$

“EXOR” function

Example

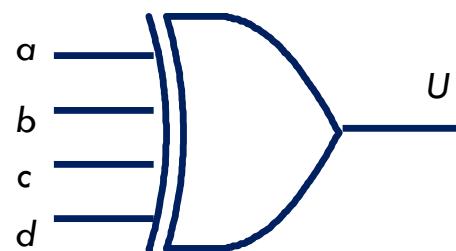

2nd solution

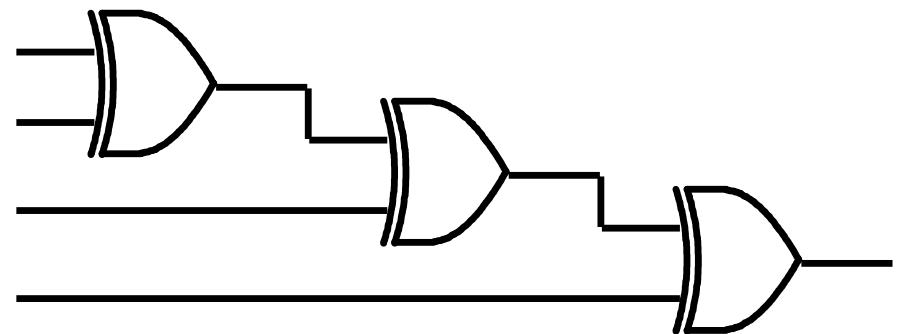

- Delay: $O(n)$
- Cost: $O(n)$

Karnaugh map for a 4-inputs exor

		ab	00	01	11	10
		cd	00	01	11	10
		00	0	1	0	1
		01	1	0	1	0
		11	0	1	0	1
		10	1	0	1	0
exor (a,b,c,d)						

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as *Boolean Primitives*, have been defined, each identified by a unique name, become a world-wide de-facto standard.
- They include:
 - not
 - and
 - or
 - nand
 - nor
 - exor
 - **exnor**

“EXNOR” function

Informal definition


- The EXOR function on 2 (or more) input variables provides the value 1 iff *an even #* of its input variables get the value 1.

Representations


- $x \odot y$
- $\text{exnor}(x,y)$

“EXNOR” function

traditional symbol

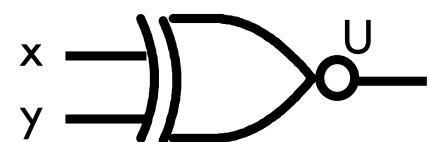

IEEE symbol

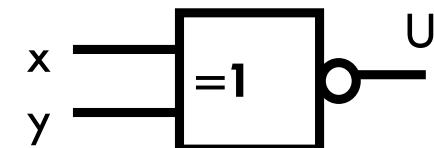

“EXNOR” function

52

Remark

$$\text{exnor}(x,y) = (\text{exor}(x,y))'$$

Complete sets of logic primitives

Question

- Is it possible to represent any Boolean Function resorting to a whatever subset of the basic functions seen so far?

Answer

- No: you have to carefully select the subset!

Examples of Complete sets

- and, or, not
- and, not
- or, not
- nand
- nor
- ...

Outline

55

- Combinational devices:
 - Basic Boolean Functions & Logic Gates
- Sequential devices:
 - Flip-Flops
 - Scannable Flip-Flops

Flip-Flop

- A flip-flop is a single-bit storage device implemented as a Moore machine.

Moore vs Mealy machines

57

Moore machine

- An FSM whose output values are determined only by its current state.

Mealy machine

- An FSM whose (Mealy) output values are determined both by its current state and by the values of its inputs.


FF classification w.r.t. data inputs

- According to their behavior w.r.t. data inputs, flip-flops are usually classified as:
 - D
 - SR
 - JK
 - T

D-type Flip-Flop

59

- Is the most widely used FF

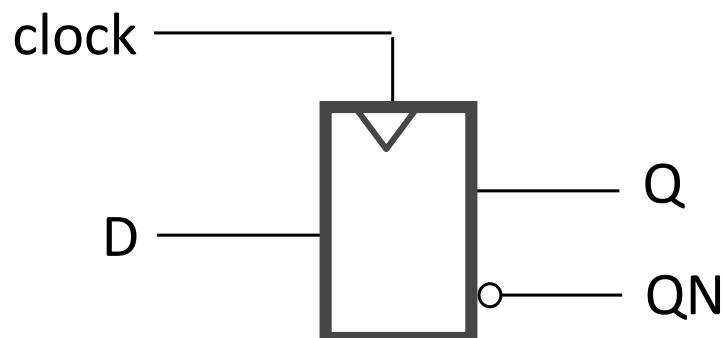


D	Q
0	0
1	1

Caveat

- Distinction between data inputs and control inputs is context and application dependent.

Example: (D = data input)


- At any clock, it stores the input data

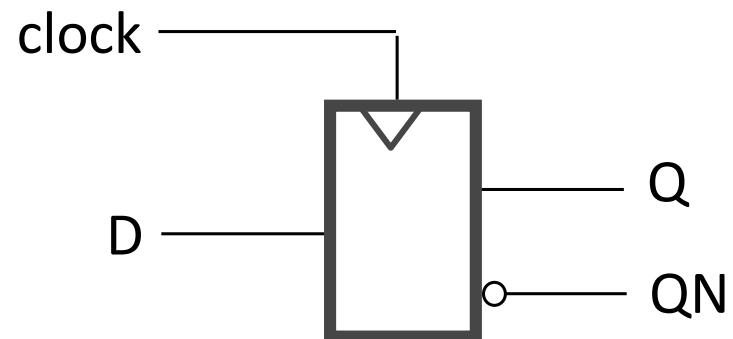

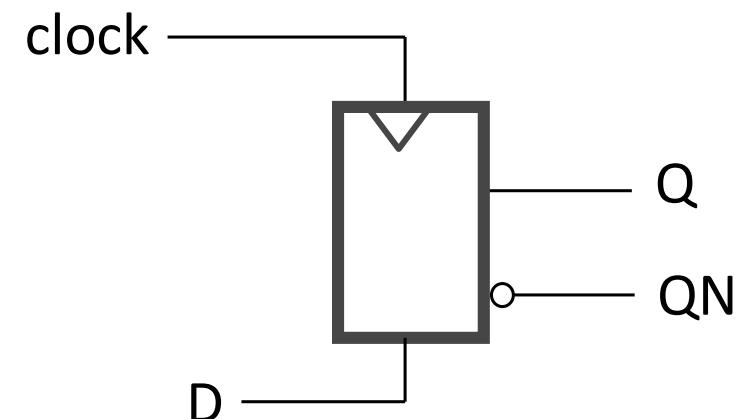Example: (D = control input)

- At any clock:

```
if (D = 0)
    then force Q=0
    else force Q=1
end if
```



Additional FF types

- In addition to the D-type FF, other ones have been proposed (namely: *JK*, *SR*, and *T*) but they are practically no longer used, due to testability reasons.

Outline

64


- Combinational devices:
 - Basic Boolean Functions & Logic Gates
- Sequential devices:
 - Flip-Flops
 - Scan Flip-Flops

Scan Flip-Flops

- In order to improve testability, most of today cell libraries include *Scan Flip-Flops*, i.e., modified versions of the D-type FF designed to make easier their inclusion into the so-called *Scan chains*.

Scan Flip-Flop


Normal_Scan_n

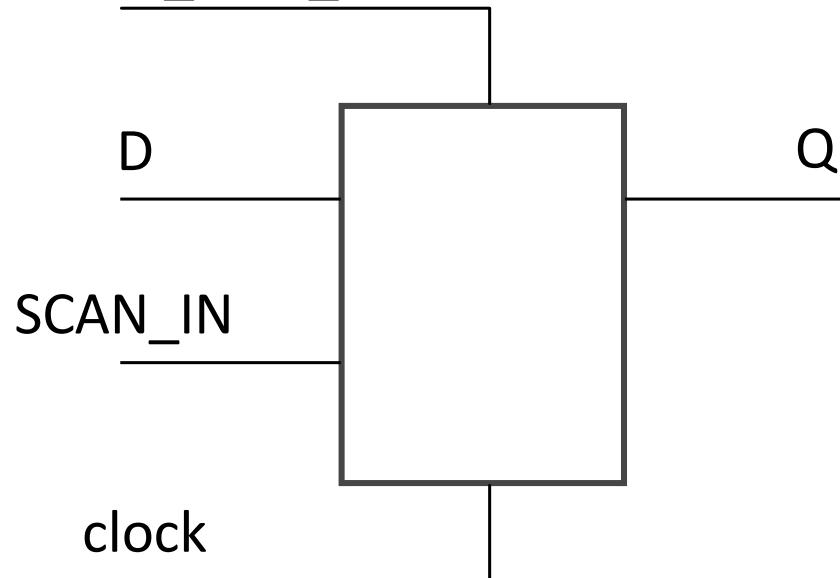

c

Scan Flip-Flop


Normal_Scan_n

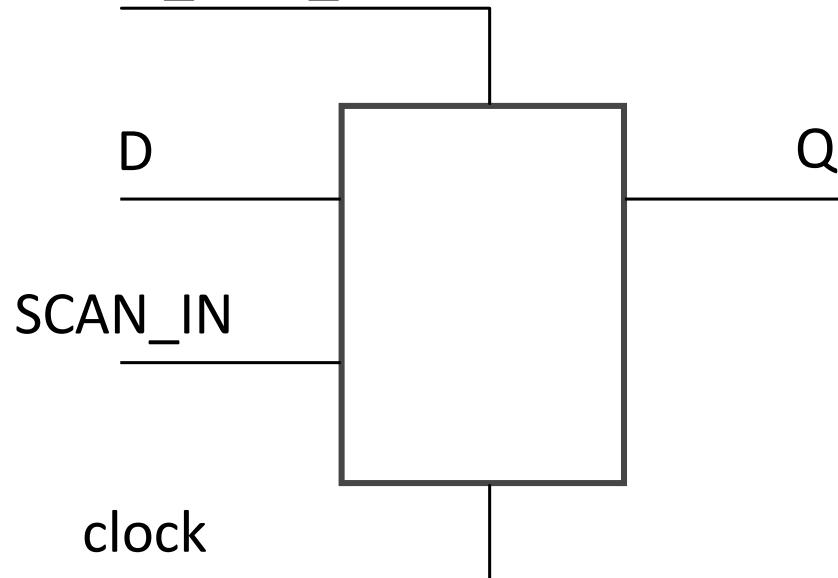

```
architecture scan_ff_arch of scan_ff is
begin
    process(clk, rst)
    begin
        if rst='1' then
            Q <= '0';
        elsif rising_edge(clk) then
            if Normal_Scan_n = '1' then
                Q <= D;
            else
                Q <= SCAN_IN;
            end if;
        end if;
    end process;
end scan_ff_arch;
```



Scan Flip-Flop

Normal_Scan_n

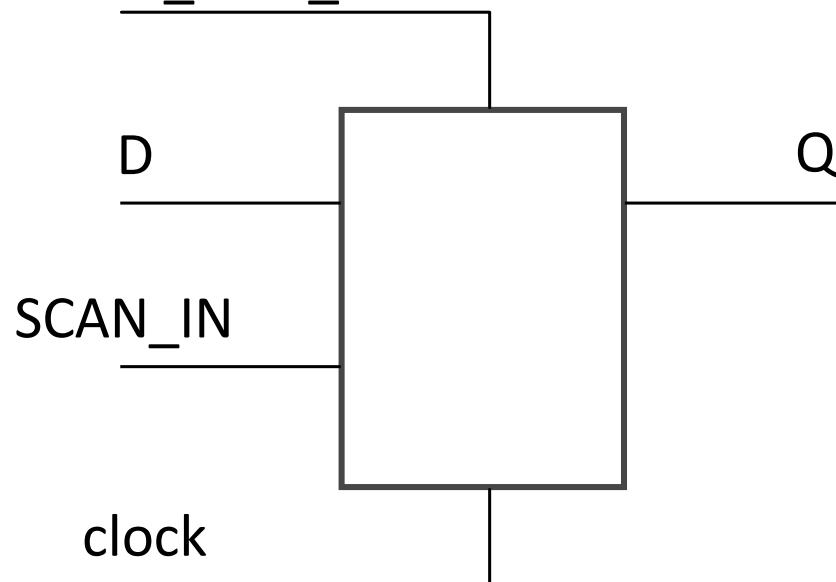

```
architecture scan_ff_arch of scan_ff is
begin
    process(clk, rst)
    begin
        if rst='1' then
            Q <= '0';
        elsif rising_edge(clk) then
            if Normal_Scan_n = '1' then
                Q <= D;
            else
                Q <= SCAN_IN;
            end if;
        end if;
    end if;
    end process;
end scan_ff_arch;
```

Scan Flip-Flop – Internal structure

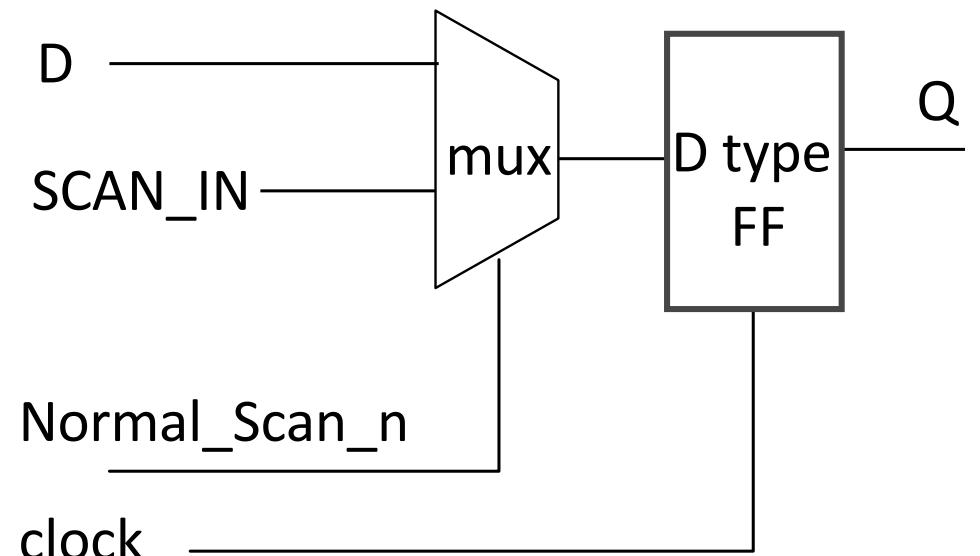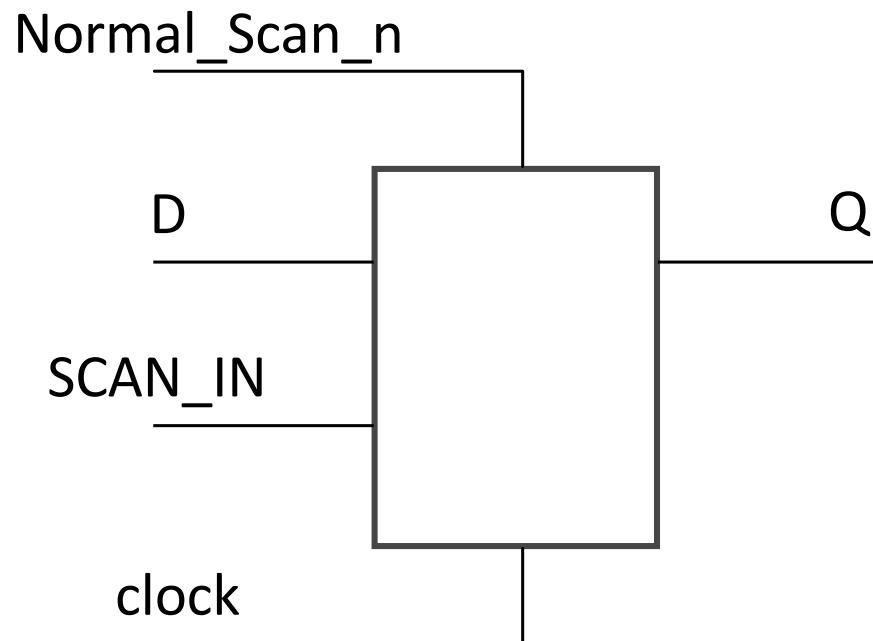


Usage

70

- An analysis of the motivations of the adoption of Scan FFs and of their usage to improve testability is introduced in lecture:
 - *HT#1 – Hardware testing - Basic concepts*

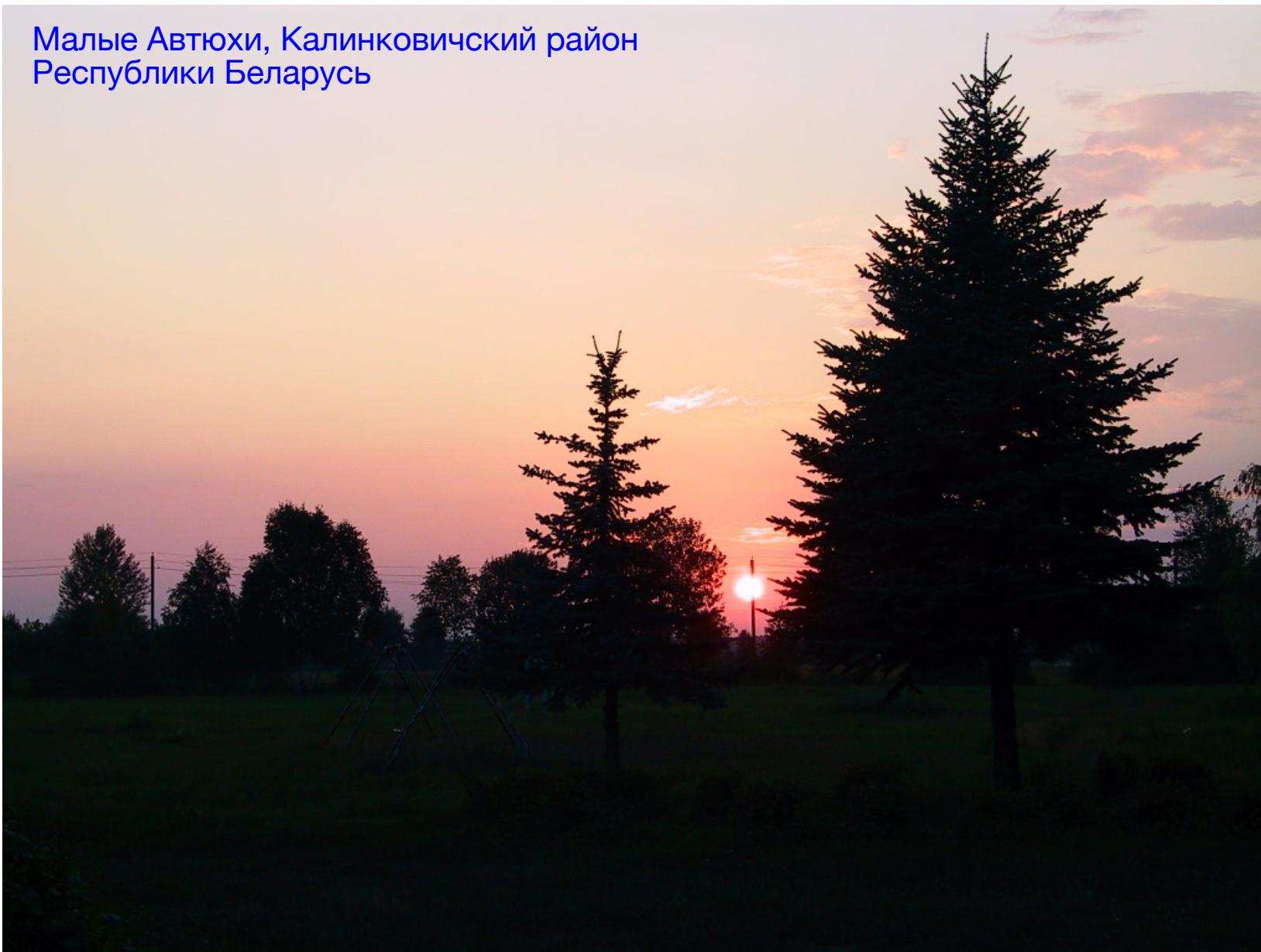Малые Автюхи, Калинковичский район
Республики Беларусь



Paolo PRINETTO

Director
CINI Cybersecurity
National Laboratory
Paolo.Prinetto@polito.it
Mob. +39 335 227529



<https://cybersecnatlab.it>